



Paper Circuits are low-voltage electronic circuits created using conductive copper tape, LEDs, and a coin-cell battery as a power source.

The circuit must be complete in order for the LED to light up. Can you find the opening?

Clear tape is used to secure the battery and LEDs to the paper.

Paper Circuits are low-voltage electronic circuits created using conductive copper tape, LEDs, and a coin-cell battery as a power source.

The circuit must be complete in order for the LED to light up. Can you find the opening?

Clear tape is used to secure the battery and LEDs to the paper.

